Electronics

Assessment:1

1.

Choose the correct Answer.

- Diode
- Triode
- Relay ✓
- Transistor

2.

Choose the correct Answer.

- Chemistry
- Mechanical
- Optical
- Electrical

3.

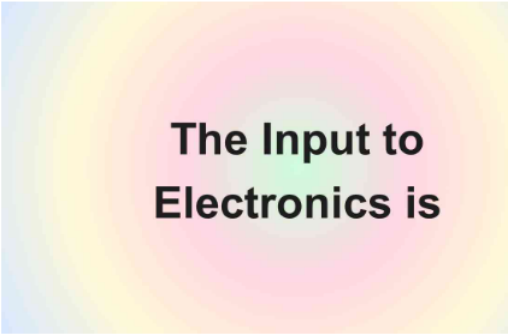

Choose the correct Answer.

- Electrical Power
- Light signal
- Electrical Signal ✓
- Sound Signal

4.

Choose the correct Answer.

- Electrical Signal ✓
- Sound Signal

5.

Choose the correct Answer.

- Vacuum Tube ✓
- Transistor

6.

Choose the correct Answer.

- Transistor
- Triode
- Diode ✓
- SCR

7.

Choose the correct Answer.

- Diode
- Transistor
- Triode ✓
- SCR

8.

Choose the correct Answer.

- Computers
- Communication

9.

Choose the correct Answer.

GATES

Amplifiers

10.

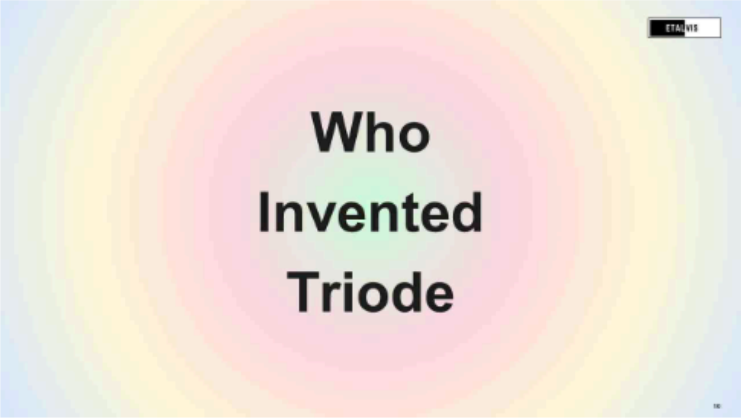

Choose the correct Answer.

Fleming

Faraday

Le De Forest ✓

Margoni

Assessment:2

1.

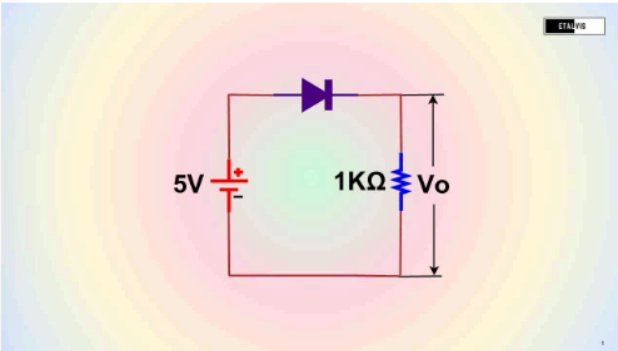

What is the Vo voltage?

- 5V
- 0V
- 4.3V ✓
- 4V

2.

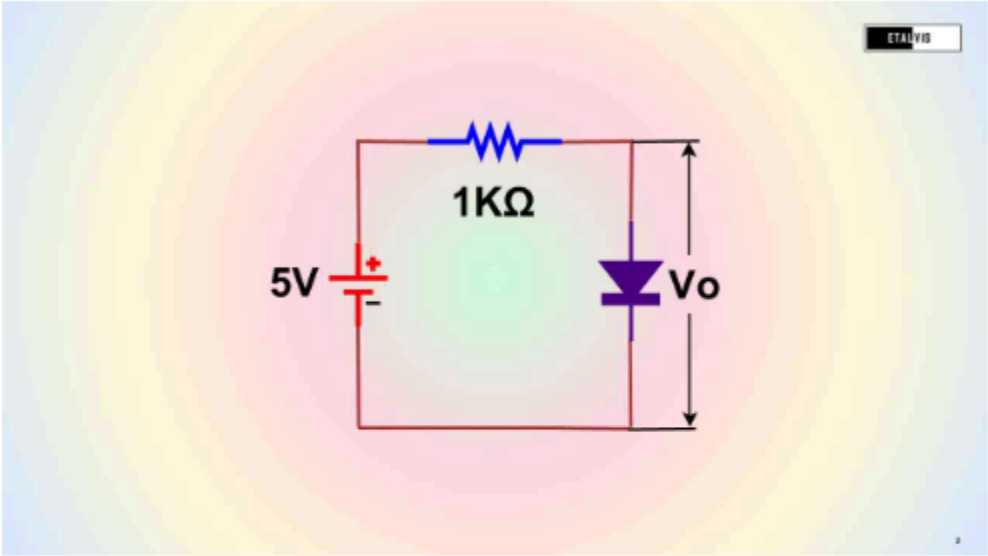

What is the Vo voltage

- 0V
- 5V
- 0.7V ✓
- 1V

3.

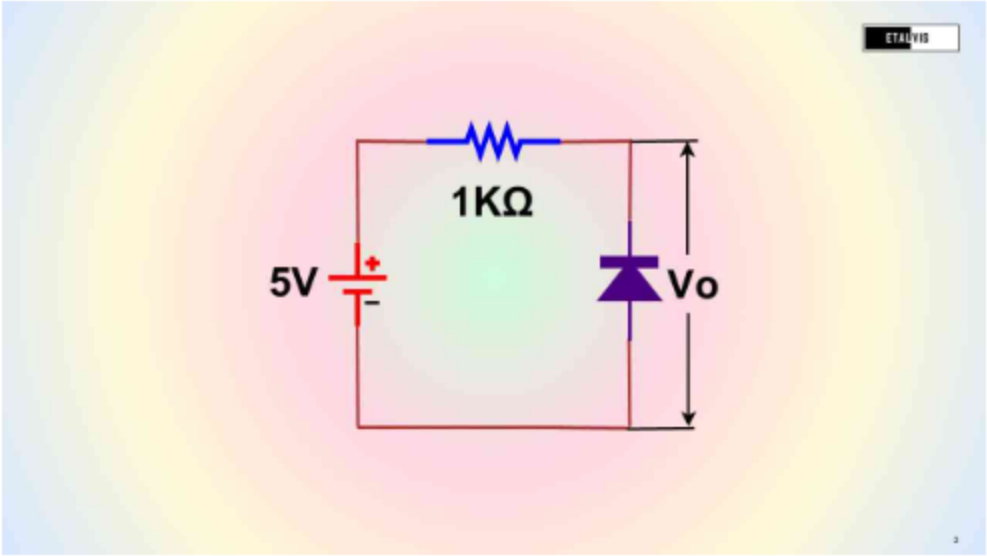

What is the Vo voltage?

0V ✗

5V

4.

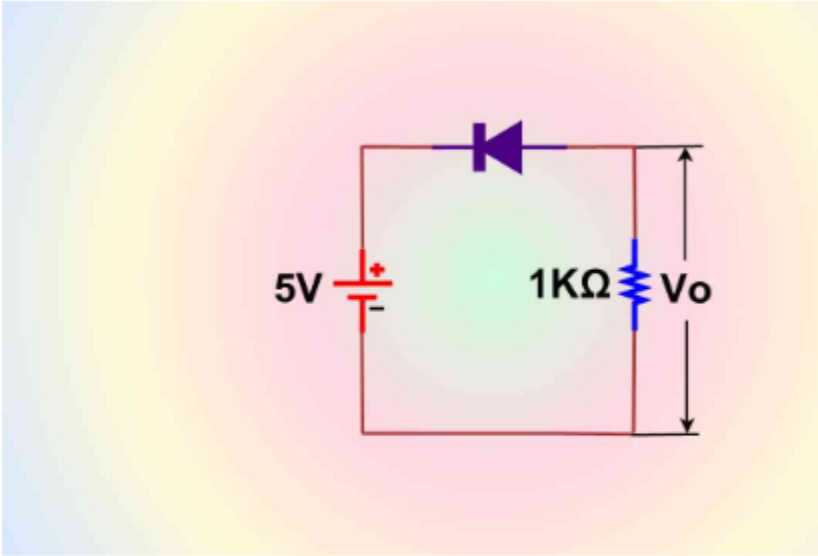

What is the Vo voltage?

0V ✓

5V

5.

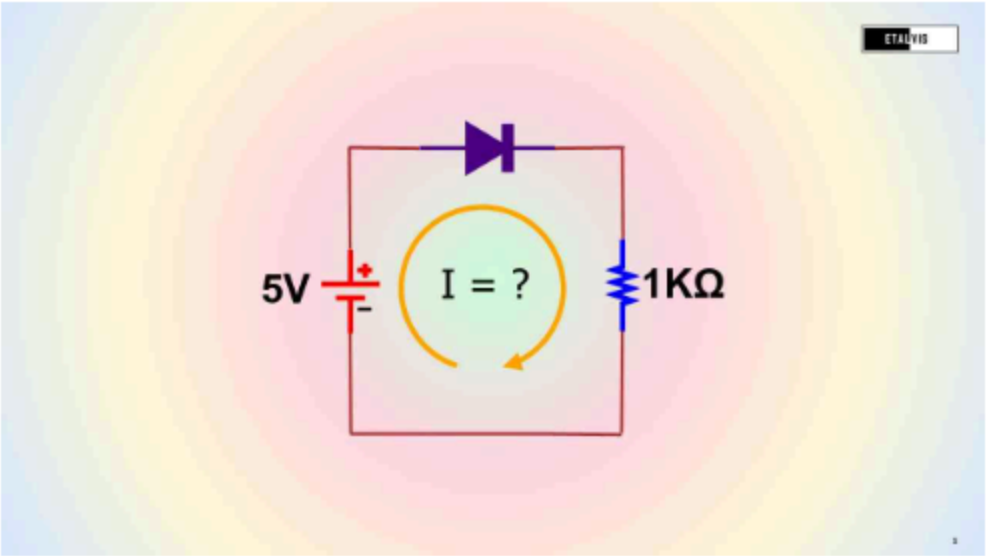

What is the value of Current I?

1mA	5mA
4.3mA ✓	0.7mA

6.

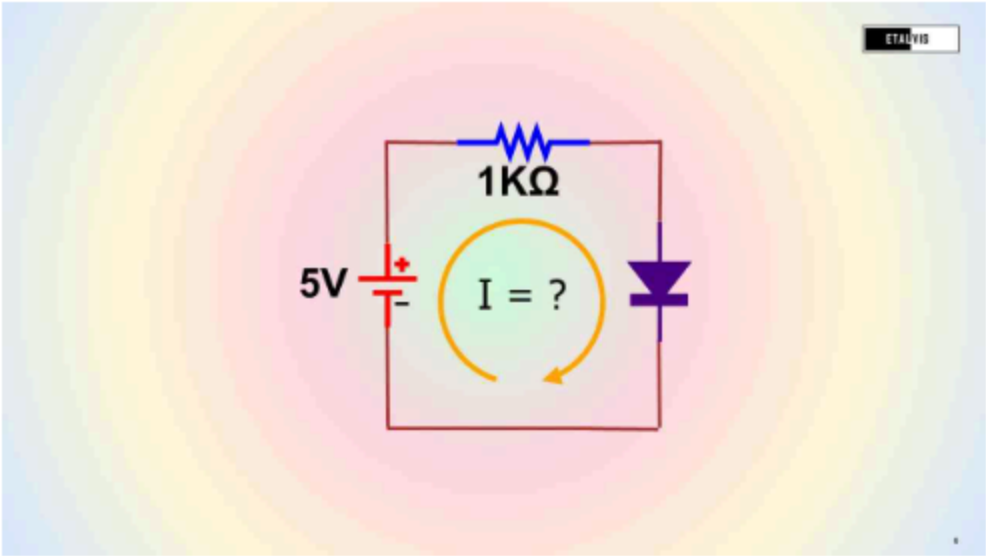

What is the value of Current I?

0mA ✗	5mA
4.3mA ✓	0.7mA

7.

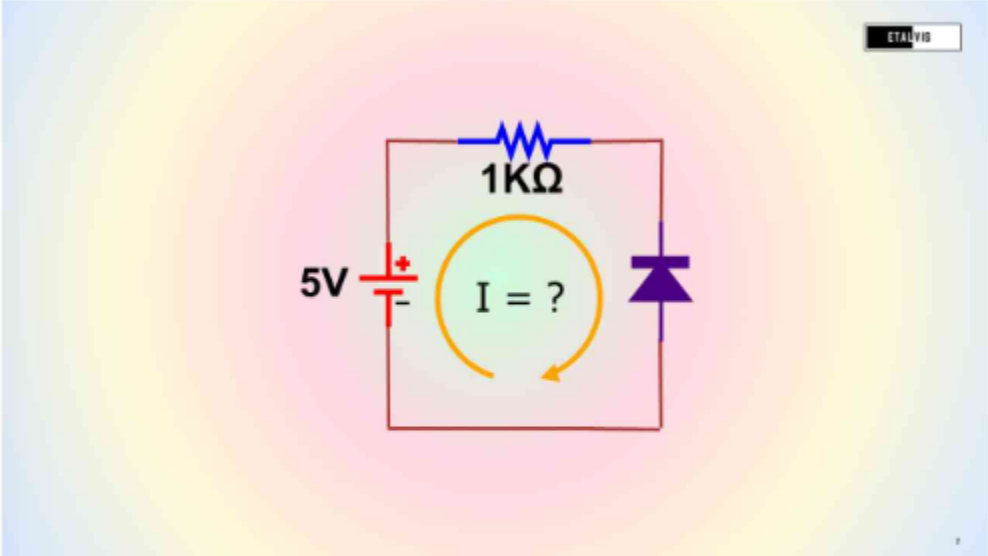

What is the value of Current I?

0mA ✓	5mA

8.

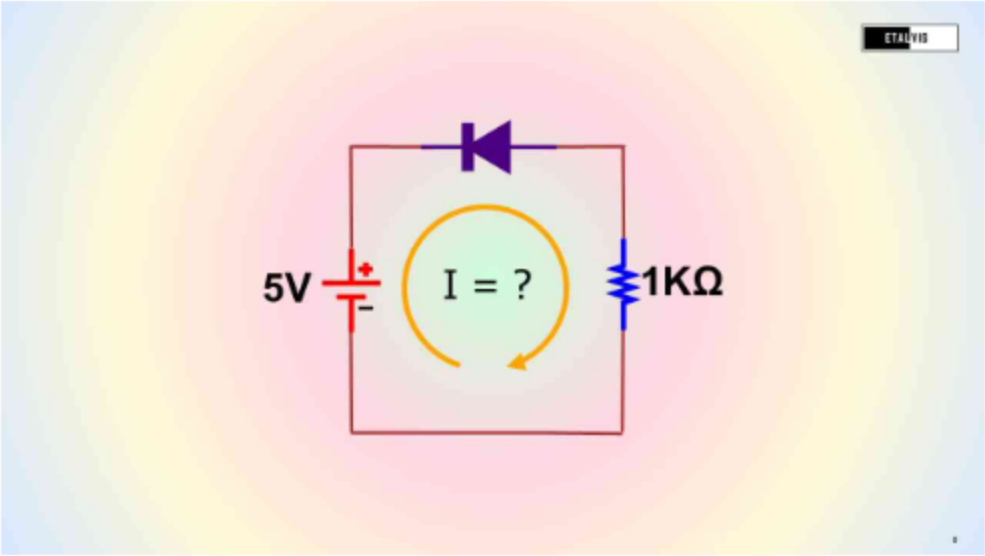

Mc

What is the value of Current I?

- 0A ✓
- 5A

9.

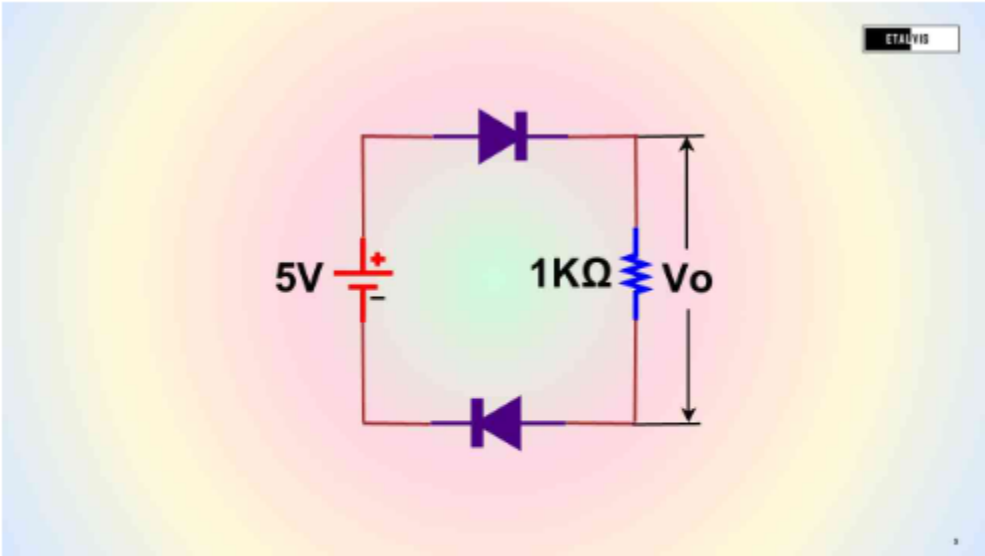

What is the Vo Voltage?

- 1.4V
- 3.6V

10.

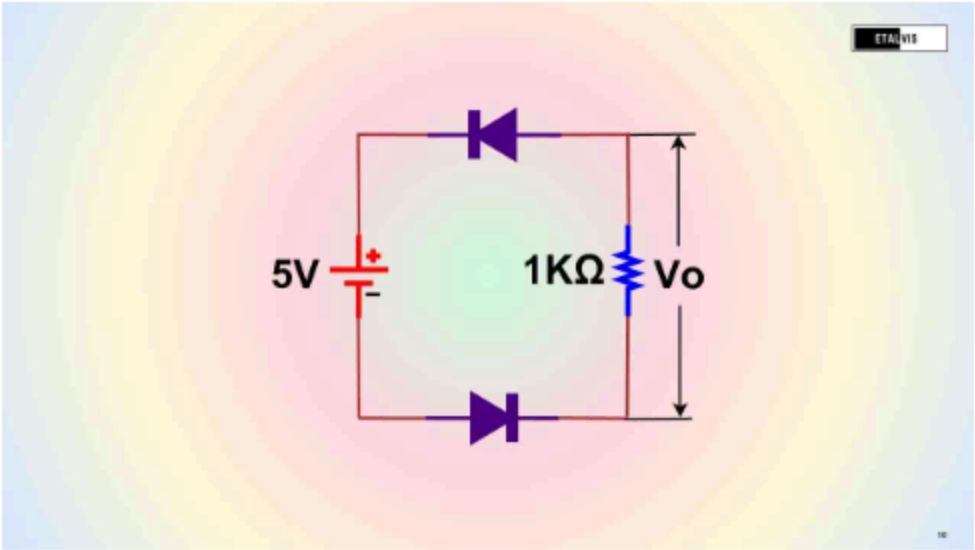

What is the Vo Voltage

1.4V	3.6V
0V ✓	5V

Assessment:3

1.

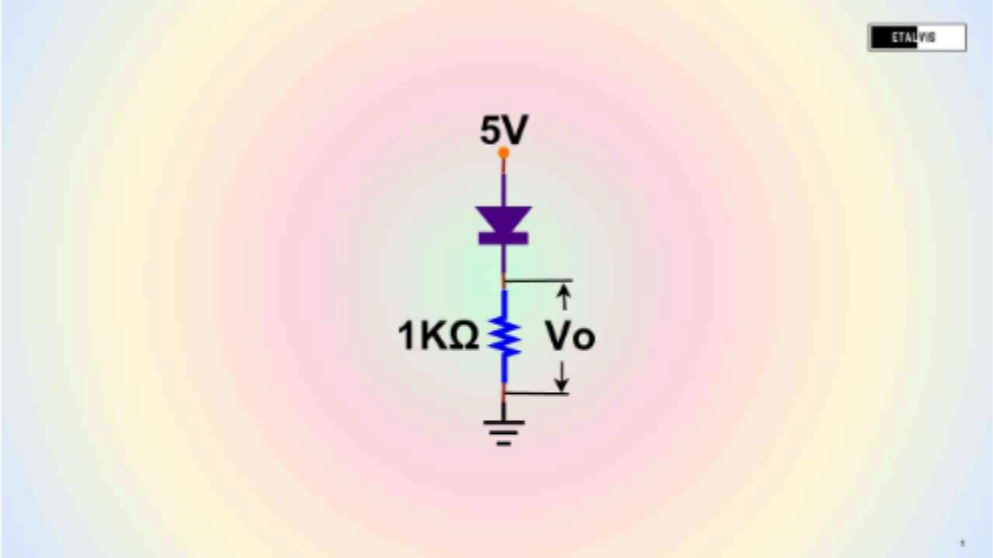

Ma

What is the value of Vo voltage?

5V	0V
0.7V	4.3V

2.

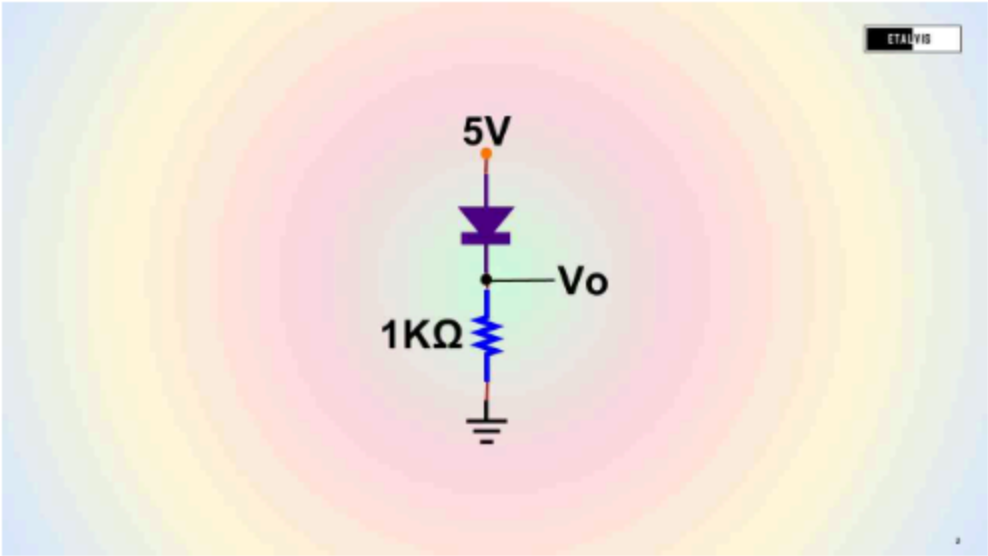

What is the value of Vo voltage?

- 5V
- 0V
- 0.7V
- 4.3V

3.

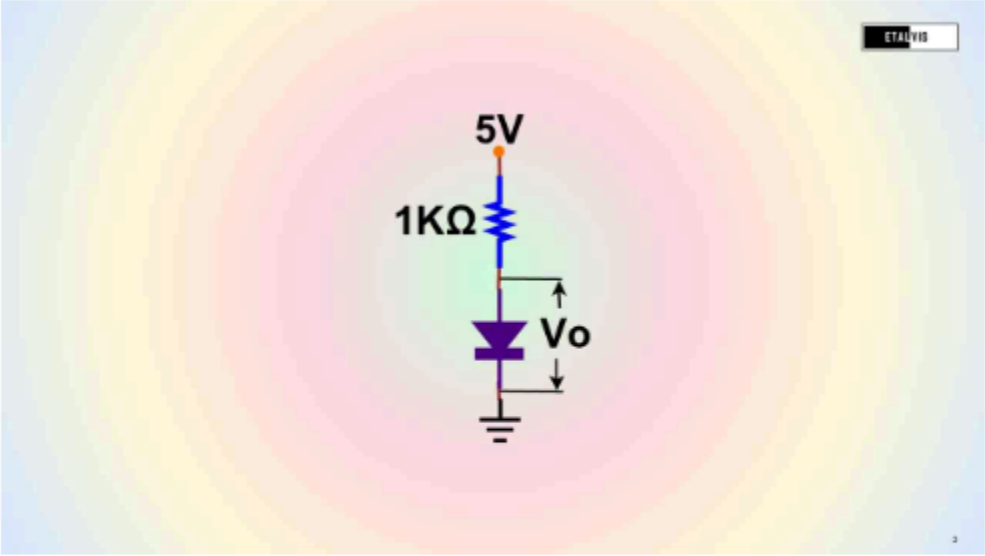

What is the value of Vo voltage?

- 5V
- 0V
- 0.7V ✓
- 4.3V

4.

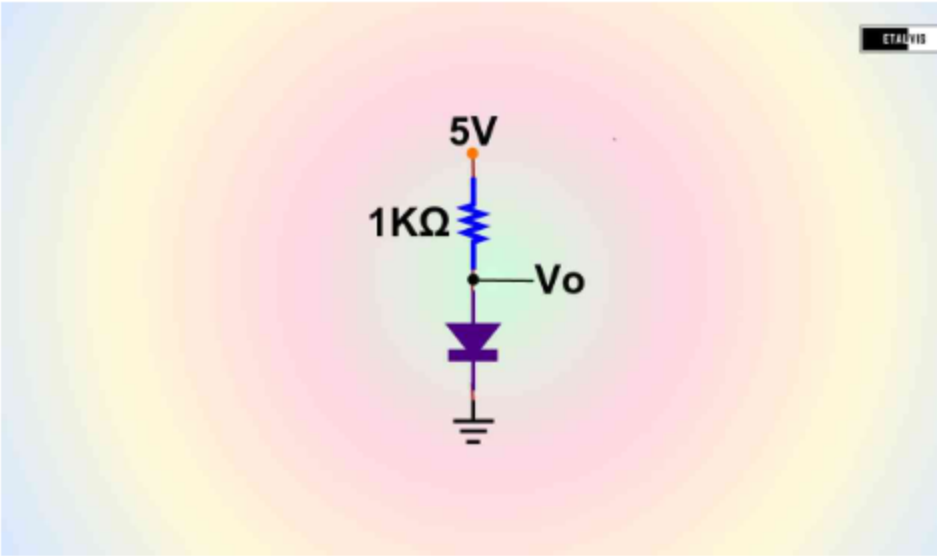

What is the value of Vo voltage?

5V	0V
0.7V ✓	4.3V

5.

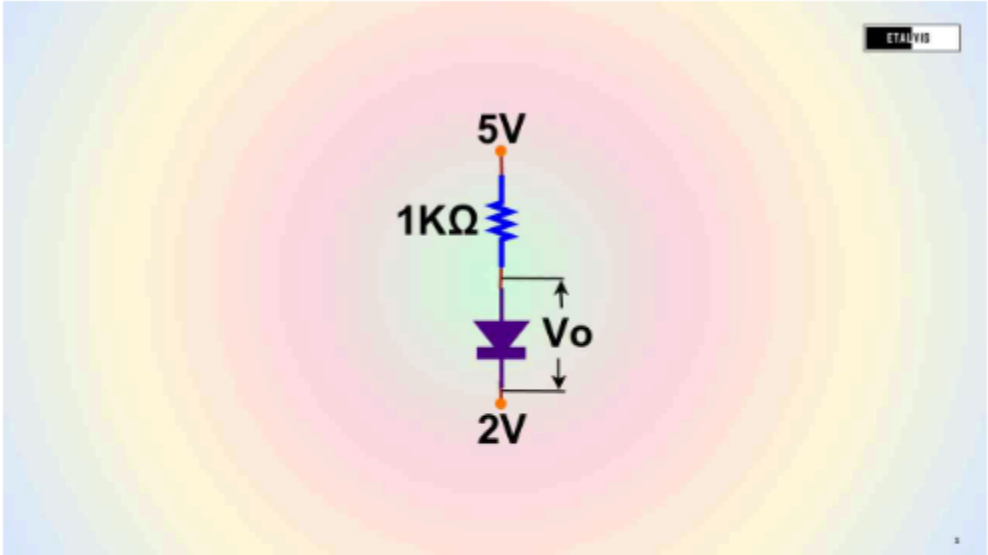

What is the value of Vo voltage?

5V	0V
0.7V ✓	4.3V

6.

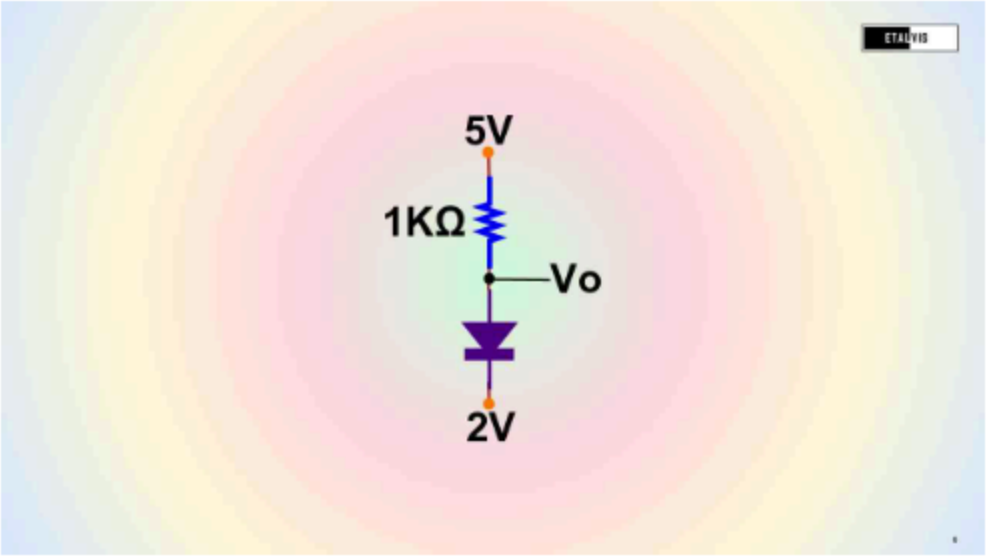

What is the value of Vo voltage?

- 4.3V
- 0.7V
- 2.7V ✓
- 5V

7.

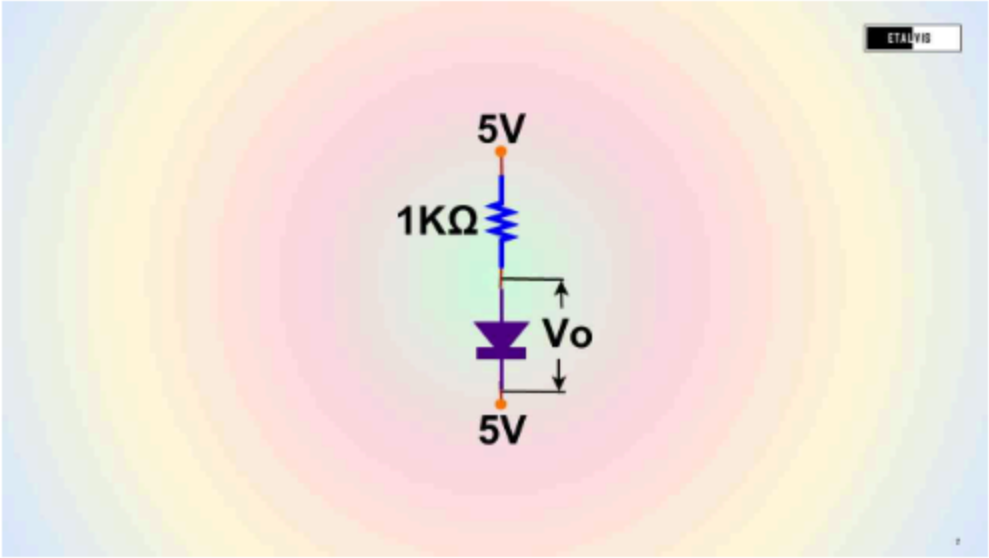

What is the value of Vo voltage?

- 5V
- 0V
- 0.7V
- 4.3V

8.

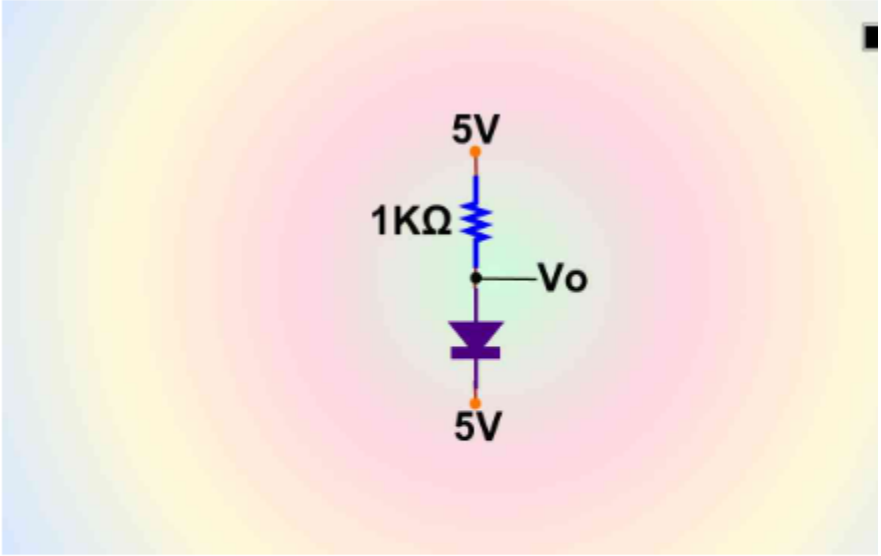

What is the value of Vo voltage?

- 5V ✓
- 0V

9.

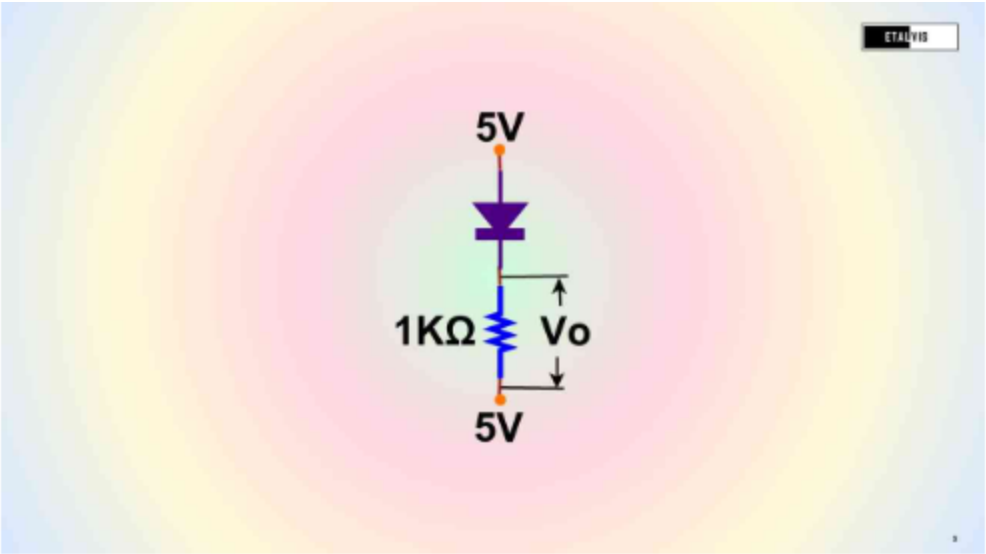

Marks:

What is the value of Vo voltage?

5V

0V ✓

10.

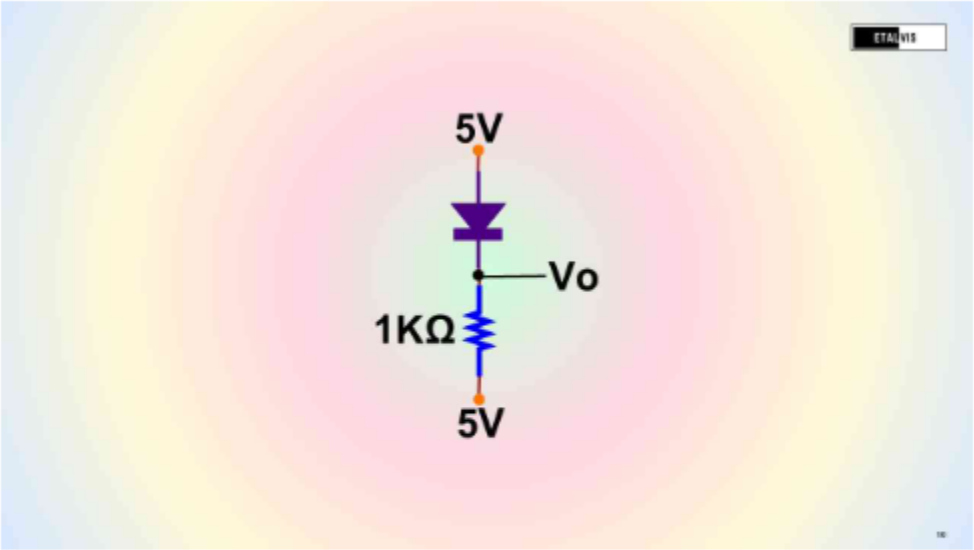

What is the value of Vo voltage?

5V ✓

0V

Assessment:4

1.

Choose the correct answer.

- Current controlled device ✓
- Voltage controlled device

2.

Choose the correct answer.

- a BJT ✓
- a FET

3.

Choose the correct answer.

- a BJT ✓
- a FET

4.

Choose the correct answer.

- current controlled device
- Voltage controlled device

5.

Choose the correct answer.

- SiO_2 as an Insulator ✓
- Phospher a an Insulator

6.

Choose the correct answer.

- True ✓
- False

7.

Choose the correct answer.

TRUE ✓

FALSE